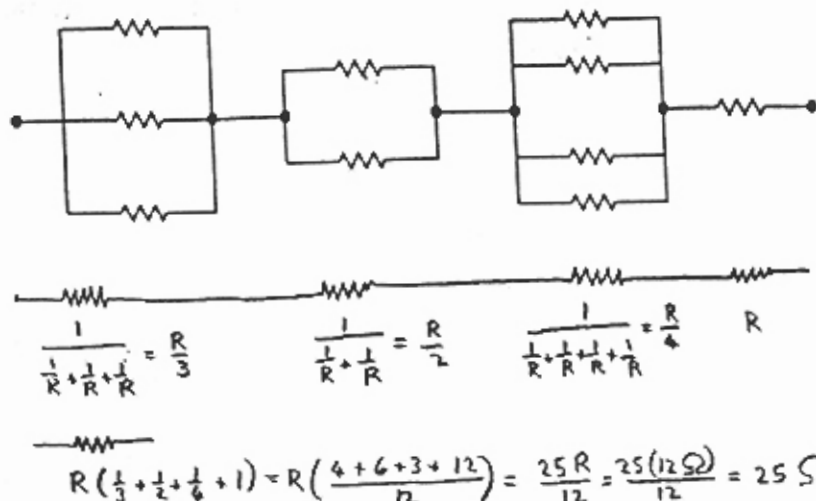


1. (10 points) Each of the resistors in the diagram is $12\ \Omega$. The resistance of the entire circuit is:

- (A) () $5.76\ \Omega$
 (B) () $25\ \Omega$
 (C) () $48\ \Omega$
 (D) () $120\ \Omega$
 (E) () None of these



Physics 241
 Exam II
 March 27, 2002.
 Solutions - Codrington

2. (10 points) In the circuit shown, the capacitor is initially uncharged. $V = 9$ Volts. At time $t = 0$, switch S is closed. If τ denotes the time constant, the approximate current through the $3\ \Omega$ resistor when $t = \tau/100$ is:

- (A) () $3/8$ A
 (B) () $1/2$ A
 (C) () $3/4$ A
 (D) () 1 A
 (E) () $3/2$ A

Final voltage across capacitor is same as case where resistors are not present (resistors only slow rate at which battery can load charge onto capacitor).

Final charge on cap. is

$$q_f = CV$$


$$q(t) = q_f(1 - e^{-t/\tau})$$

$$i(t) = \frac{dq}{dt} = \frac{q_f}{\tau} e^{-t/\tau} \quad \text{where } \tau = C(R_1 + R_2)$$

$$= \frac{(CV)}{C(R_1 + R_2)} e^{-(\tau/100)/\tau}$$

$$= \frac{V}{R_1 + R_2} e^{-1/100}$$
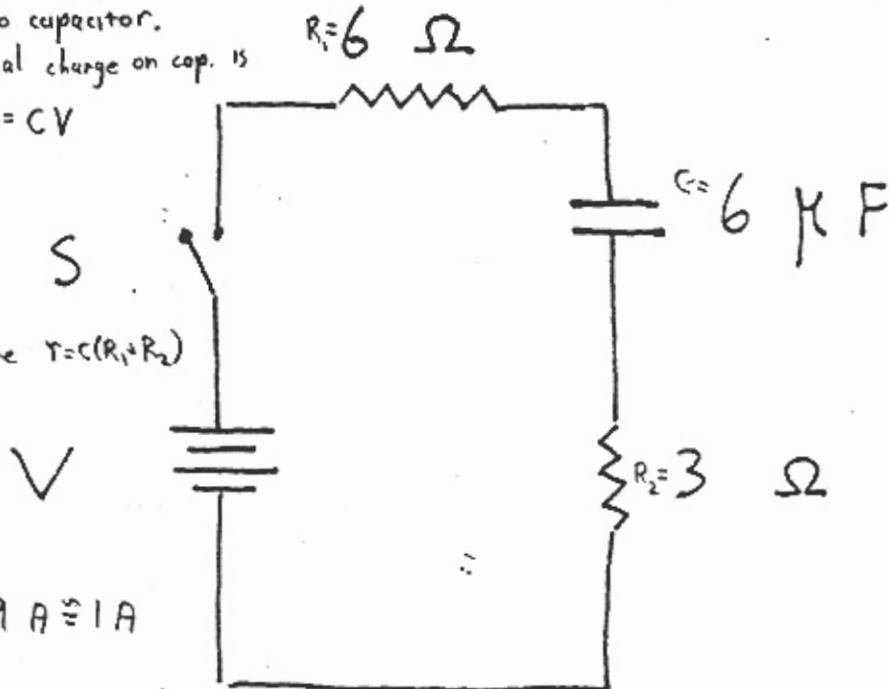
$$= \frac{9\text{V}}{6 + 3\ \Omega} e^{-1/100} = .99\text{ A} \approx 1\text{ A}$$



3. (10 points) At one instant an electron (charge = -1.6×10^{-19} C) is moving in the xy plane, the components of its velocity being $v_x = 5 \times 10^5$ m/s and $v_y = 3 \times 10^5$ m/s. A magnetic field of 0.8 T is in the positive z direction. At that instant the magnitude of the magnetic force on the electron is:

- (A) () 0
 (B) () 3.8×10^{-14} N
 (C) () 5.1×10^{-14} N
 (D) () 6.4×10^{-14} N
 (E) () 7.5×10^{-14} N

$$\vec{B} = .8\ \hat{k}\ \text{T} \quad \vec{v} = 5 \times 10^5 \hat{i} + 3 \times 10^5 \hat{j} \quad \text{m/s}$$

$$\vec{v} \times \vec{B} = (5\hat{i} + 3\hat{j}) \times (.8\hat{k}) \times 10^5$$


$$= 4\hat{i} \times \hat{k} + 2.4\hat{j} \times \hat{k} \times 10^5 \quad \text{T} \cdot \frac{\text{m}}{\text{s}}$$

$$|\vec{F}| = |q| |\vec{v} \times \vec{B}| = (1.6 \times 10^{-19}) (\sqrt{(2.4)^2 + (-4)^2} \times 10^5)$$

$$= 7.46 \times 10^{-14}\ \text{N}$$

4. (10 points) A loop of wire carrying a current of 2.0 A is in the shape of a right triangle with two equal sides, each 15 cm long. A 0.7 T uniform magnetic field is in the plane of the triangle and is perpendicular to the hypotenuse. The resultant magnetic force on the two sides has a magnitude of:

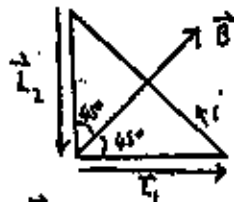- (A) () 0
 (B) () 0.21 N
 (C) () **0.30 N**
 (D) () 0.41 N
 (E) () 0.51 N




$$\vec{F} = i\vec{L}_1 \times \vec{B} + i\vec{L}_2 \times \vec{B} = iL_1 B \sin 45^\circ \text{ (out of page)} + iL_2 B \sin 135^\circ \text{ (out of page)}$$

$$|\vec{F}| = \frac{2}{\sqrt{2}} iLB = \sqrt{2} (2.0 \text{ A})(.15 \text{ m})(.7 \text{ T}) = .297$$

5. (10 points) Two parallel wires, 4 cm apart, carry currents of 2 A and 4 A respectively, in opposite directions. The force per unit length in N/m of one wire on the other is:

Let \vec{L} be a vector pointing out of the page representing a length of wire 2

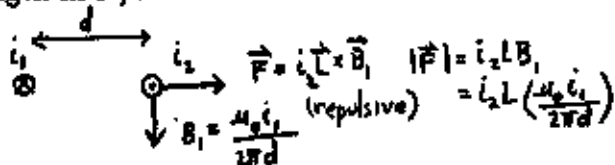- (A) () 1×10^{-3} , repulsive
 (B) () 1×10^{-3} , attractive
 (C) () **4×10^{-5} , repulsive**
 (D) () 4×10^{-5} , attractive
 (E) () none of these



$$\frac{|\vec{F}|}{L} = \frac{\mu_0 i_1 i_2}{2\pi d} = \frac{(4\pi \times 10^{-7} \text{ T}\cdot\text{m/A})(2 \text{ A})(4 \text{ A})}{2\pi (.04 \text{ m})} = 4.0 \times 10^{-5} \text{ N repulsive.}$$

6. (10 points) Two long straight wires enter a room through a window. One carries a current of 3.0 A into the room while the other carries a current of 5.0 A out. The magnitude in T·m of the path integral $\oint \vec{B} \cdot d\vec{s}$ around the window frame is:

- (A) () 2.5×10^{-8}
 (B) () 3.8×10^{-8}
 (C) () 6.3×10^{-8}
 (D) () 1.0×10^{-5}
 (E) () none of these




$$\oint \vec{B} \cdot d\vec{s} = \mu_0 (i_1 - i_2)$$

$$|\oint \vec{B} \cdot d\vec{s}| = |\mu_0 (i_1 - i_2)| = \mu_0 |i_1 - i_2|$$

$$= (4\pi \times 10^{-7} \text{ T}\cdot\text{m/A}) |3 - 5 \text{ A}| = 2.51 \times 10^{-6} \frac{\text{T}\cdot\text{m}}{\text{A}}$$

7. (10 points) A single loop of wire with a radius of 7.5 cm rotates about a diameter in a uniform magnetic field of 1.6 T. The axis of rotation is perpendicular to the magnetic field. To produce a maximum emf of 1.0 V, it should rotate at:

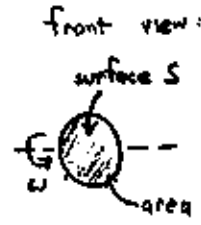- (A) () 0
 (B) () 2.7 rad/s
 (C) () 5.6 rad/s
 (D) () **35 rad/s**
 (E) () 71 rad/s



Flux thru area A

$$\Phi_B = \int_S \vec{B} \cdot d\vec{A}$$

$$= \int_S |\vec{B}| dA \cos \theta$$

$$= \int_S |\vec{B}| dA \cos \omega t$$

$$= |\vec{B}| \cos \omega t \int_S dA$$

$$= |\vec{B}| A \cos \omega t$$

$$\mathcal{E} = - \frac{d}{dt} (N \Phi_B) = - \frac{d}{dt} (1 |\vec{B}| A \cos \omega t) = - |\vec{B}| A (-\omega \sin \omega t) = |\vec{B}| A \omega \sin \omega t$$

max |E|

$$\Rightarrow \text{max } |\mathcal{E}| = |\vec{B}| A \omega = |\vec{B}| (\pi r^2) \omega$$

$$\Rightarrow \omega = \frac{\text{max } |\mathcal{E}|}{|\vec{B}| \pi r^2} = \frac{1.0 \text{ V}}{(1.6 \text{ T}) \pi (.075 \text{ m})^2} = 35.36 \frac{\text{rad}}{\text{s}}$$

8. (10 points) A 6.0 mH inductor and a 3.0 Ω resistor are wired in series to a 12 V ideal battery. A switch in the circuit is closed at time 0, at which time the current is zero. 2.0 ms later the energy stored in the inductor is:

Final current is same as when inductor is not present $\Rightarrow i_f = \frac{12 \text{ V}}{3 \Omega} = 4 \text{ A}$

For series LR circuit

- (A) () 0
 (B) () $1.92 \times 10^{-2} \text{ J}$
 (C) () $1.1 \times 10^{-3} \text{ J}$
 (D) () $1.8 \times 10^{-3} \text{ J}$
 (E) () $2.2 \times 10^{-3} \text{ J}$

$$i(t) = i_f (1 - e^{-t/\tau_L}) \quad \text{where } \tau_L = \frac{L}{R}$$

$$= i_f (1 - e^{-Rt/L}) = (4.0 \text{ A}) (1 - e^{-(3 \Omega)(2 \times 10^{-3} \text{ s}) / (6 \times 10^{-3} \text{ H})})$$

$$= 2.528 \text{ A}$$

$$U = \frac{1}{2} L i^2 = \frac{1}{2} (6.0 \times 10^{-3} \text{ H}) (2.528 \text{ A})^2 = 1.917 \times 10^{-2} \text{ J}$$

9. (10 points) An LC circuit has a capacitance of 30 μF and an inductance of 15 mH. At time $t = 0$ the charge on the capacitor is 10 μC and the current is 20 mA. The maximum current is:

- (A) () 18 mA
 (B) () 20 mA
 (C) () 25 mA
 (D) () 35 mA
 (E) () 42 mA

initial energy $U_0 = \frac{1}{2} L i_0^2 + \frac{1}{2} \frac{q_0^2}{C}$
 = energy when all energy is stored in inductor
 = $\frac{1}{2} L i^2$

$$\Rightarrow \frac{1}{2} L i^2 = \frac{1}{2} L i_0^2 + \frac{1}{2} \frac{q_0^2}{C} \Rightarrow i^2 = i_0^2 + \frac{q_0^2}{LC}$$

$$\Rightarrow i = \sqrt{i_0^2 + \frac{q_0^2}{LC}} = \left((20 \times 10^{-3} \text{ A})^2 + \frac{(10 \times 10^{-6} \text{ C})^2}{(15 \times 10^{-3} \text{ H})(30 \times 10^{-6} \text{ F})} \right)^{1/2} = .0249 \text{ A}$$

10. (10 points) What resistance R should be connected in series with an inductance $L = 220 \text{ mH}$ and capacitance $C = 12.0 \mu\text{F}$ for the maximum charge on the capacitor to decay to 99.0% of its initial value in 50.0 cycles? (Assume $\omega' \approx \omega$.)

$$q(t) = Q e^{-Rt/2L} \cos(\omega't + \phi). \quad \text{We take } \omega' \approx \omega = \frac{1}{\sqrt{LC}}$$

- (A) () $4.33 \times 10^{-2} \Omega$
 (B) () $4.33 \times 10^{-3} \Omega$
 (C) () $6.35 \times 10^{-4} \Omega$
 (D) () $8.66 \times 10^{-3} \Omega$
 (E) () $9.57 \times 10^{-3} \Omega$

Decay is due to $e^{-Rt/2L}$ term.

Find R such that $e^{-Rt/2L} = .99$

ω' has units $\frac{\text{rad}}{\text{sec}}$. $\omega' = 2\pi f' \Rightarrow f' = \frac{\omega'}{2\pi} \frac{\text{cycles}}{\text{sec}}$

Period $T = \frac{1}{f'} = \frac{2\pi}{\omega'} \frac{\text{sec}}{\text{cycle}}$

Time for N cycles is $t = NT = N \left(\frac{2\pi}{\omega'} \right) = \frac{2\pi N}{\omega} = \frac{2\pi N}{\frac{1}{\sqrt{LC}}} = 2\pi N \sqrt{LC}$

$$e^{-Rt/2L} = .99 \Rightarrow e^{-\frac{R}{2L} (2\pi N \sqrt{LC})} = .99 \Rightarrow -\frac{R (2\pi N \sqrt{LC})}{2L} = \ln(.99)$$

$$\Rightarrow R = -\frac{\sqrt{L} \ln(.99)}{\pi N \sqrt{C}} = -\frac{\sqrt{(220 \times 10^{-3} \text{ H})} \ln(.99)}{\pi (50.0 \text{ cycles}) \sqrt{(12.0 \times 10^{-6} \text{ F})}} = 8.66 \times 10^{-3} \Omega$$